

Question Paper

Exam Date & Time: 09-Jan-2023 (02:30 PM - 05:30 PM)



MANIPAL ACADEMY OF HIGHER EDUCATION


FIRST SEMESTER B.TECH. EXAMINATIONS - JANUARY 2023
SUBJECT: ELE 1071 / ELE-1071 - BASIC ELECTRICAL TECHNOLOGY

Marks: 50


Duration: 180 mins.

Answer all the questions.

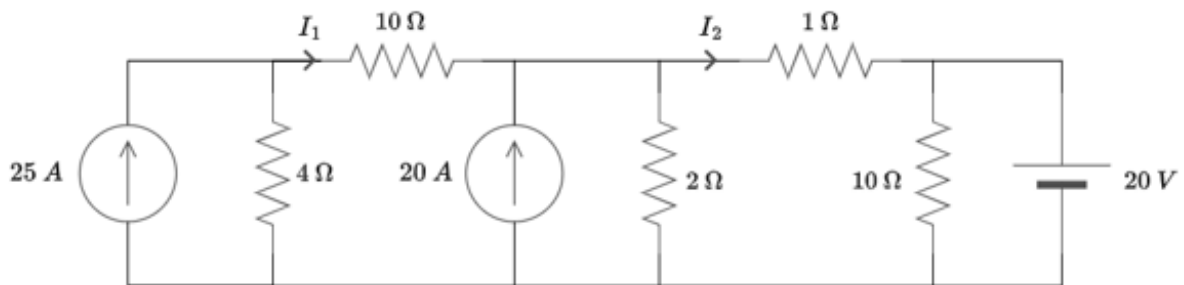
- 1A) Find the currents I_1 and I_2 in the given network. (3)



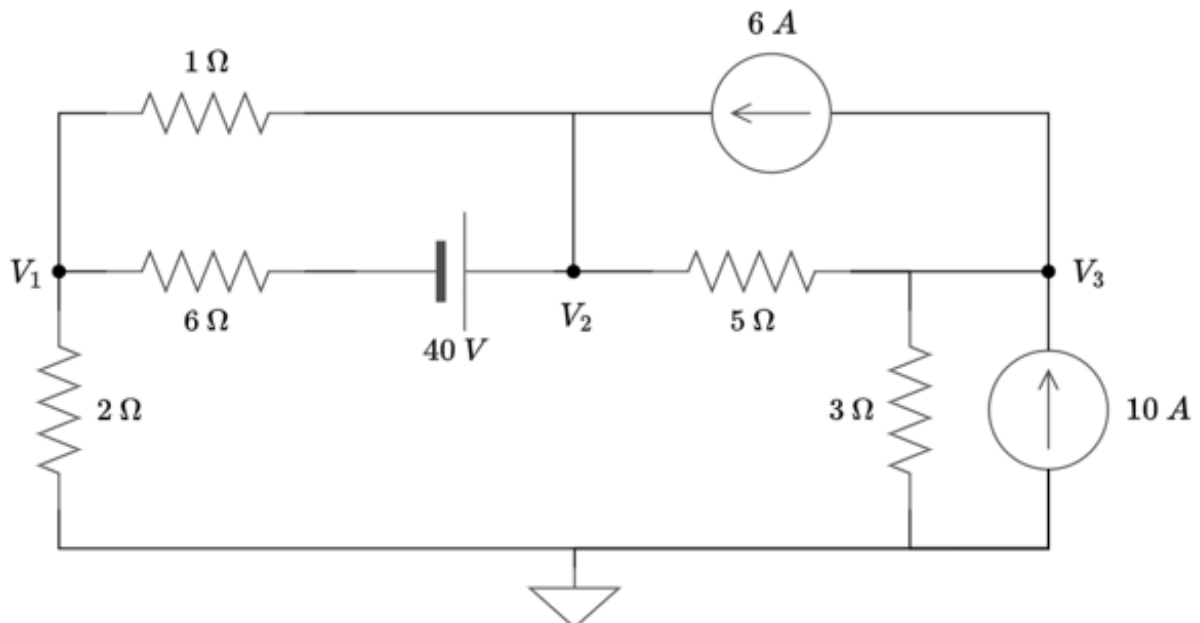
- 1B) Determine the node voltages V_1 , V_2 and V_3 in the given circuit. (3)



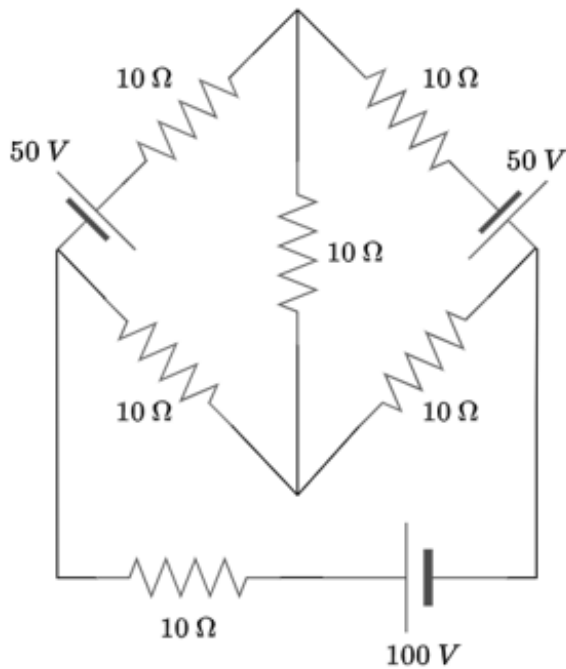
- 1C) Determine the current supplied by 100 V source to the circuit using **Thevenin's** theorem. (4)



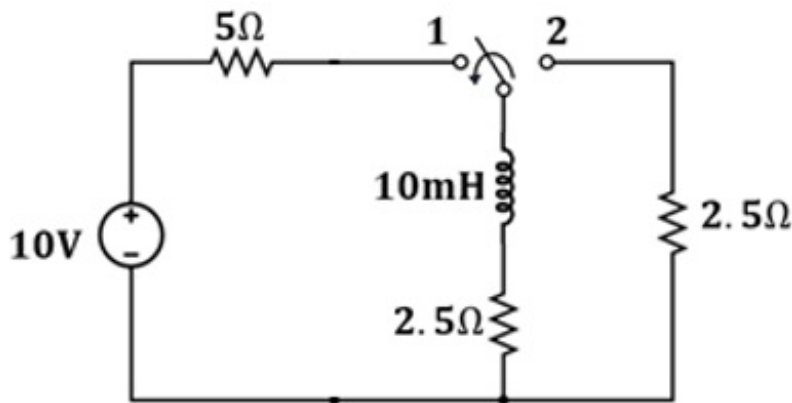
- 2A) For the network shown, the switch is closed on to position 1 at $t = 0$ and then moved to position 2 at $t = 1.4$ ms. Determine the current in the inductor when $t = 2.5$ ms. (3)




- 2B) For the magnetic circuit shown, the reluctance of the central limb (AB) is 10×10^5 AT/Wb and the reluctance of the outer limbs (ACB and ADB) are same and equal to 15×10^5 AT/Wb. The number of turns in the coil is 1000. Central limb AB has flux density of 1.25 Tesla and a mean length of 10 cm. Assuming uniform area of cross section, determine (4)
- The current to be flowing in the coil to produce 0.5 mWb in limb ADB.
 - The relative permeability of the magnetic material.

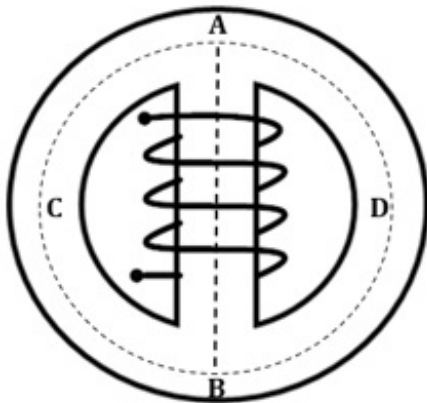

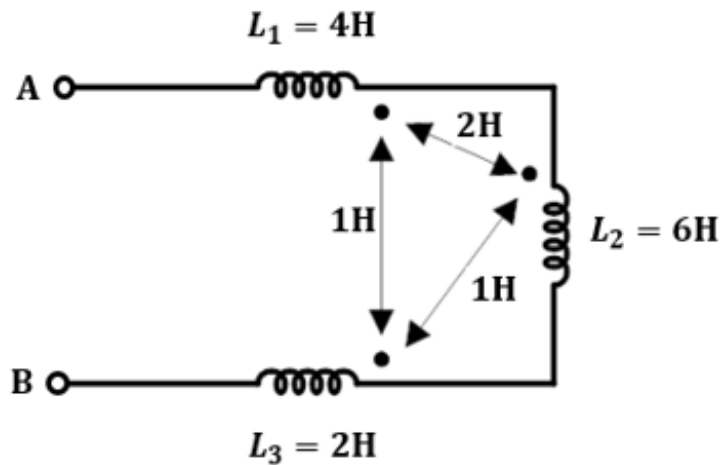- 2C) Determine the equivalent inductance seen at terminals A & B in the given network. Also compute the coupling coefficients k_{12} , k_{23} and k_{13} . (3)



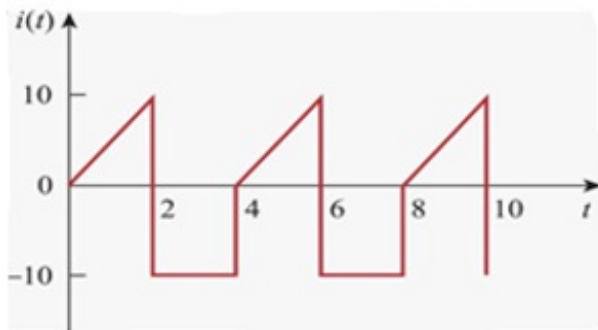- 3A) Determine the **RMS** value of the current waveform shown. If the current is passed through a resistor of $10\ \Omega$, find the power absorbed by the resistor. (3)



- 3B) A metal-filament lamp, rated at **250 W, 100 V**, is to be connected in series with a capacitor across a **230 V, 50 Hz** supply. Calculate: (a) the capacitance of the capacitor, and (b) the phase angle between the circuit current and the supply voltage. (4)
- 3C) A circuit having a resistance of **12 Ω** , an inductance of **0.15 H** and a capacitance of **100 μF** in series, is connected across a **100 V, 50 Hz** supply. Calculate: (a) the impedance, (b) the current, (c) the voltages across **R, L** and **C**, and (d) the circuit power factor. (3)
- 4A) A **1-phase** AC generator supplies the following loads: (4)
 i) Lighting load of **20 kW** at **unity** power factor.
 ii) Induction motor load of **100 kW** at **0.707** lagging power factor.
 iii) Synchronous motor load of **50 kW** at **0.9** leading.
 Calculate the total **kW** and **kVA** delivered by the generator and the power factor at which it works.
- 4B) Three similar coils, each having a resistance of **8 Ω** and an inductive reactance of **8 Ω** are connected in **star** across a **415 V, 3-phase, 50 Hz** supply. Calculate active, reactive, and apparent power of the load and individual wattmeter readings if the power is measured by two-wattmeter method. (6)
- 5A) A star-connected balanced load is supplied from a **3-phase** supply with a line voltage of **416 V** at a frequency of **50 Hz**. Each phase of the load consists of a resistance and a capacitor connected in series, and the readings on two-wattmeters connected to measure the total power supplied are **782 W** and **1980 W**. Calculate: (4)
 a) The power factor of the circuit
 b) The line current.
 c) The capacitance of each capacitor.
- 5B) With a neat schematic discuss the working principle of a 1-phase digital energy meter. (3)
- 5C) Using circuit representation classify the different types of DC motors. Discuss their features. (3)

-----End-----